

Components and Sequential Circuits

Martin Schoeberl

Technical University of Denmark
Embedded Systems Engineering

February 16, 2023

Overview

- ▶ Vending machine project
- ▶ Repeat combinational building blocks
- ▶ Power user II
- ▶ Components and top-level
- ▶ Sequential circuits

Admin

- ▶ How is the lab work going so far? Too easy?
- ▶ Continue to organize yourself in groups of 2–3
 - ▶ 1 is also OK
 - ▶ You can ask for finding a group via slack (in channel general)
- ▶ There is a group defined in Learn to register
 - ▶ You have to show parts of the Vending Machine to a TA
 - ▶ In the week that follows the exercise
 - ▶ On time: full points, one week late: half the points
- ▶ Next week guest lecture by Jens on timing

A Vending Machine from 1952



Source: Minnesota Historical Society, [CC BY-SA 2.0](https://creativecommons.org/licenses/by-sa/2.0/)

The Vending Machine

- ▶ Final project is a vending machine
- ▶ Detailed specification document will be given
 - ▶ Put into the public in chisel-lab
- ▶ Inputs: coins, buy
- ▶ Display: price and current amount
- ▶ Output: release can or error
- ▶ Small challenge to multiplex the display
- ▶ State machine with data path is the *brain* of the VM
- ▶ Guided step by step over several weeks

Vending Machine Specification I

- ▶ Sell 1 item and not returning any money
- ▶ Set price with 5 switches (1–31 kr.)
- ▶ Display price on two 7-segment displays (hex.)
- ▶ Accept 2 and 5 kr. (two push buttons)
- ▶ Display sum on two 7-segment displays (hex.)
 - ▶ Amount entered so far
- ▶ Does not return money, left for the next purchase

Vending Machine Specification II

- ▶ Push button *Buy*
 - ▶ If not enough money, activate *alarm* as long as buy is pressed
 - ▶ If enough money, activate *release item* for as long as *buy* is pressed and reduce *sum* by the price of the item
- ▶ Optional extras (for a 12)
 - ▶ Display decimal numbers
 - ▶ Supplement alarm by some visuals (e.g., blinking display)
 - ▶ Count coins and display an alarm when compartment is full (> 20 coins)
 - ▶ Have some text scrolling on the display
 - ▶ Supplement alarm with some audio
 - ▶ Talk to the user
 - ▶ ...
 - ▶ Your ideas :-)

Design and Implementation

- ▶ Implementation shall be a state machine plus datapath
- ▶ Design your datapath on a sheet of paper
- ▶ Datapath
 - ▶ Does add and subtract
 - ▶ Contains a register to hold the sum
 - ▶ Needs some multiplexer to operate
- ▶ Display needs multiplexing
 - ▶ Implemented with some counters and a multiplexer
- ▶ Show each part of your design to a TA
 - ▶ 7-segment decoder, 7-segment with a counter, display multiplexer, complete vending machine

Vending Machine Design and Implementation Steps

- ▶ We start in week 6
 - ▶ Hexadecimal to 7-segment decoder
 - ▶ 7-segment display with a counter
 - ▶ Multiplexed Seven-Segment Display
 - ▶ Testing the Vending Machine
 - ▶ Complete Vending Machine
- ▶ *Show steps and your final working design to a TA*

Final Report

- ▶ One report per group
- ▶ A single PDF
 - ▶ Your group number is part of the file name (e.g., group7.pdf)
 - ▶ Code as listing in an appendix (no .zip files)
 - ▶ Hand in in DTU Learn
- ▶ Content
 - ▶ Abstract
 - ▶ Preface (Who did what)
 - 1. Introduction and Problem Formulation
 - 2. Analysis and Design
 - 3. Implementation
 - 4. Testing
 - 5. Results
 - 6. Discussion
 - 7. Conclusion
 - ▶ List of References
 - ▶ Appendix: Chisel code

Questions on Final Project?

Combinational Circuit with Conditional Update

- ▶ Value first needs to be wrapped into a `Wire`
- ▶ Updates with the Chisel update operation `:=`
- ▶ With `when` we can express a conditional update
- ▶ The condition is an expression with a Boolean result
- ▶ The resulting circuit is a multiplexer
- ▶ The rule is that the last enabled assignment counts
 - ▶ Here the order of statements has a meaning

```
val enoughMoney = Wire(Bool())
```

```
enoughMoney := false.B  
when (coinSum >= price) {  
  enoughMoney := true.B  
}
```

Comparison

- ▶ The usual operations (as in Java or C)
 - ▶ Unusual equal and unequal operator symbols
 - ▶ To keep the original Sala operators usable for references
- ▶ Operands are UInt and SInt
- ▶ Operands can be Bool for equal and unequal
- ▶ Result is Bool

>, >=, <, <=
===, !=

Boolean Logical Operations

- ▶ Operands and result are Bool
- ▶ Logical NOT, AND, and OR

```
val notX = !x
val bothTrue = a && b
val orVal = x || y
```

The “Else” Branch

- ▶ We can express a form of “else”
- ▶ Note the `.` in `.otherwise`

```
val w = Wire(UInt())
```


```
when (cond) {  
  w := 1.U  
} .otherwise {  
  w := 2.U  
}
```

A Chain of Conditions

- ▶ To test for different conditions
- ▶ Select with a priority order
- ▶ The first expression that is true counts
- ▶ The hardware is a chain of multiplexers

```
val w = Wire(UInt())
```
 
```
when (cond) {  
  w := 1.U  
} .elsewhen (cond2) {  
  w := 2.U  
} .otherwise {  
  w := 3.U  
}
```



Default Assignment

- ▶ Practical for complex expressions
- ▶ Forgetting to assign a value on all conditions
 - ▶ Would describe a latch
 - ▶ Runtime error in Chisel
- ▶ Assign a default value is good practise

```
val w = WireDefault(0.U)
```

```
when (cond) {
```

```
  w := 3.U
```

```
}
```


```
// ... and some more complex conditional  
  assignments
```

Logic Can Be Expressed as a Table

- ▶ Sometimes more convenient
- ▶ Still combinational logic (gates)
- ▶ Is converted to Boolean expressions
- ▶ Let the synthesize tool do the conversion!
- ▶ We use the `switch` statement

```
switch (sel) {  
  is ("b00".U) { result := "b0001".U}  
  is ("b01".U) { result := "b0010".U}  
  is ("b10".U) { result := "b0100".U}  
  is ("b11".U) { result := "b1000".U}  
}
```

A Decoder

 


- ▶ Converts a binary number of n bits to an m -bit signal, where $m \leq 2^n$
- ▶ The output is one-hot encoded (exactly one bit is one)
- ▶ Building block for a m -way Mux
- ▶ Used for address decoding in a computer system
- ▶ Maybe of use for the display multiplexer

Truth Table of a Decoder

a	b
00	0001
01	0010
10	0100
11	1000

An Encoder

 

- ▶ Converts one-hot encoded signal
- ▶ To binary representation

Truth Table of an Encoder

a	b
0001	00
0010	01
0100	10
1000	11
????	??

- ▶ Only defined for one-hot input

Encoder in Chisel

- ▶ We cannot describe a function with undefined outputs
- ▶ We use a default assignment of "b00"

```
b := "b00".U
switch (a) {
  is ("b0001".U) { b := "b00".U}
  is ("b0010".U) { b := "b01".U}
  is ("b0100".U) { b := "b10".U}
  is ("b1000".U) { b := "b11".U}
}
```

Power User II

- ▶ Every craftsmen starts with good-quality tools
- ▶ “Tools amplify your talent”¹
 - ▶ The better your tools, the more productive you are
 - ▶ The better you know them, the more productive you are
- ▶ IDEs (Eclipse, IntelliJ) are nice, I love them too
- ▶ But we shall go beyond it
- ▶ Use tools (and write your own)
- ▶ Help with: google, man pages, or even plain `–help` (or `-h`)
- ▶ <https://www.oreilly.com/learning/ten-steps-to-linux-survival>
 - ▶ This is about command line tools, not just Linux

¹The Pragmatic Programmer: From Journeyman to Master, by Andrew Hunt and David Thomas

Power User II

- ▶ Use the command line, shell, terminal
- ▶ In Windows: PowerShell
 - ▶ You may want to install the Linux subsystem
- ▶ Universal Unix commands (Windows, Mac, Linux)
- ▶ Navigating the file system:
 - ▶ Change directory: `cd`
 - ▶ Print working directory: `pwd`
 - ▶ Make a directory: `mkdir abc`
 - ▶ Create a file: `echo test > abc.txt`
 - ▶ Show file content: `cat abc.txt`
 - ▶ Remove a file: `rm abc.txt`
- ▶ Run your Chisel code with `sbt run`
- ▶ You used the terminal already from within IntelliJ ;-)

Power User II

- ▶ We talked about `git` last week
- ▶ To version your source
- ▶ Maybe hosting on GitHub
- ▶ Most teaching material is on GitHub
- ▶ Use `git pull` to update the lab material
- ▶ Show how to use it, now!
 - ▶ Clone a repo: `git clone path`
 - ▶ Get the newest version: `git pull`
 - ▶ Further commands: `git commit`, `push`, `log`, `status`
 - ▶ Overview of changes: `gitk`
- ▶ There are also GUI tools available, IntelliJ includes `git` support

Structure With Bundles

- ▶ A Bundle to group signals
- ▶ Can be different types
- ▶ Defined by a class that extends Bundle
- ▶ Named fields as vals within the block
- ▶ Like a C struct or VHDL record

```
class Channel() extends Bundle {  
  val data = UInt(32.W)  
  val valid = Bool()  
}
```

Using a Bundle

- ▶ Create it with `new`
- ▶ Wrap it into a `Wire`
- ▶ Field access with *dot* notation

```
val ch = Wire(new Channel())  
ch.data := 123.U  
ch.valid := true.B  
  
val b = ch.valid
```

Write, Reg, and IO

- ▶ `UInt`, `SInt`, and `Bits` are Chisel types, not hardware
- ▶ `Wire`, `Reg`, or `IO` generates hardware
 - ▶ A `Wire` is a combinational circuit
 - ▶ A `Reg` is a register
 - ▶ A `IO` is a connection (for a module)
- ▶ Can wrap any Chisel type, also `Bundle` or `Vec`
- ▶ Give it a name by assigning it to a `val`

```
val number = Wire(UInt())  
val reg = Reg(SInt())
```

Using = or :=

- ▶ Later assign or reassign a value or expression with :=

```
number := 10.U  
reg := value - 3.U
```

- ▶ Note the small difference between = and :=
 - ▶ May be confusing to start with
- ▶ Use = when *creating* a hardware object to give it a name
- ▶ Use := when assigning or reassigning to an *existing* hardware object

Components/Modules

- ▶ Components/Modules are building blocks
 - ▶ Component and module are two names for the same thing
- ▶ Components have input and output ports (= pins)
 - ▶ Organized as a `Bundle`
 - ▶ Wrapped into an `IO()`
 - ▶ assigned to a field `io`
- ▶ We build circuits as a hierarchy of components
- ▶ In Chisel a component is called `Module`
- ▶ Components/Modules are used to organize the circuit
 - ▶ Similar to using methods in Java

Input/Output Ports

- ▶ Ports are the *interface* to a module
- ▶ Ports are bundles with directions
- ▶ Ports used to connect modules

```
class AluIO extends Bundle {  
  val function = Input(UInt(2.W))  
  val inputA = Input(UInt(4.W))  
  val inputB = Input(UInt(4.W))  
  val result = Output(UInt(4.W))  
}
```


An Adder Module

- ▶ A class that extends `Module`
- ▶ Interface (port) is a `Bundle`, wrapped into an `IO()`, and stored in the field `io`
- ▶ Circuit description in the constructor

```
class Adder extends Module {  
  val io = IO(new Bundle {  
    val a = Input(UInt(4.W))  
    val b = Input(UInt(4.W))  
    val result = Output(UInt(4.W))  
  })  
  
  val addVal = io.a + io.b  
  io.result := addVal  
}
```

Connections

- ▶ Simple connections just with assignments, e.g.,

```
adder.io.a := ina
```

```
adder.io.b := inb
```


- ▶ Note the dot access to the field `io` and then the IO field

Module Usage

- ▶ Create with `new` and wrap into a `Module()`
- ▶ Interface port via the `io` field
- ▶ Note the assignment operator `:=` on `io` fields

```
val adder = Module(new Adder())  
adder.io.a := ina  
adder.io.b := inb  
val result = adder.io.result
```

Example: Arithmetic Logic Unit

 

- ▶ Also called ALU
- ▶ A central component of a microprocessor
- ▶ Two inputs, one function select, and an output
- ▶ Part of the *datapath*


Example: Arithmetic Logic Unit

```
class Alu extends Module {
  val io = IO(new Bundle {
    val a = Input(UInt(16.W))
    val b = Input(UInt(16.W))
    val fn = Input(UInt(2.W))
    val y = Output(UInt(16.W))
  })

  // some default value is needed
  io.y := 0.U

  // The ALU selection
  switch(io.fn) {
    is(0.U) { io.y := io.a + io.b }
    is(1.U) { io.y := io.a - io.b }
    is(2.U) { io.y := io.a | io.b }
    is(3.U) { io.y := io.a & io.b }
  }
}
```

Hierarchy of Components Example

 

Components CompA and CompB

```
class CompA extends Module {  
  val io = IO(new Bundle {  
    val a = Input(UInt(8.W))  
    val b = Input(UInt(8.W))  
    val x = Output(UInt(8.W))  
    val y = Output(UInt(8.W))  
  })  
  
  // function of A  
}  
  
class CompB extends Module {  
  val io = IO(new Bundle {  
    val in1 = Input(UInt(8.W))  
    val in2 = Input(UInt(8.W))  
    val out = Output(UInt(8.W))  
  })  
  
  // function of B  
}
```

Component CompC

```
class CompC extends Module {  
  val io = IO(new Bundle {  
    val inA = Input(UInt(8.W))  
    val inB = Input(UInt(8.W))  
    val inC = Input(UInt(8.W))  
    val outX = Output(UInt(8.W))  
    val outY = Output(UInt(8.W))  
  })  
  
  // create components A and B  
  val compA = Module(new CompA())  
  val compB = Module(new CompB())  
  
  // connect A  
  compA.io.a := io.inA  
  compA.io.b := io.inA  
  io.outX := compA.io.x  
  // connect B  
  compB.io.in1 := compA.io.y  
  compB.io.in2 := io.inC
```


Chisel Main

- ▶ Create one top-level Module
- ▶ Invoke the Chisel code emitter from the App
- ▶ Pass the top module (e.g., `new Hello()`)
- ▶ Optional: pass some parameters (in an Array)
- ▶ Following code generates Verilog code for *Hello World*

```
object Hello extends App {  
  emitVerilog(new Hello())  
}
```

Hello World in Chisel

```
class Hello extends Module {
  val io = IO(new Bundle {
    val led = Output(UInt(1.W))
  })
  val CNT_MAX = (500000000 / 2 - 1).U

  val cntReg = RegInit(0.U(32.W))
  val blkReg = RegInit(0.U(1.W))

  cntReg := cntReg + 1.U
  when(cntReg === CNT_MAX) {
    cntReg := 0.U
    blkReg := ~blkReg
  }
  io.led := blkReg
}
```

Generated Verilog for Hello

- ▶ Hello is the top-level of our blinking LED
- ▶ No real need to read this code
- ▶ But pin assignment for the synthesis
- ▶ Additional pins: `clock` and `reset`
- ▶ User pin names with a leading `io_`

```
module Hello(  
    input    clock,  
    input    reset,  
    output   io_led  
);
```

Generated Verilog for Hello

- ▶ We can find our two register definitions
- ▶ @... gives Chisel source and line number (e.g., 17)

```
reg [31:0] cntReg; // @[Hello.scala 17:23]
reg [31:0] _RAND_0;
reg blkReg; // @[Hello.scala 18:23]
```

Generated Verilog for Hello

- ▶ The increment and comparison against maximum value

```
assign _T_1 = cntReg + 32'h1; // @[Hello.scala 20:20]
assign _T_2 = cntReg == 32'h2faf07f; // @[Hello.scala 21:21]
assign _T_3 = ~ blkReg; // @[Hello.scala 23:15]
assign io_led = blkReg; // @[Hello.scala 25:10]
```

Generated Verilog for Hello

- ▶ Verilog register code

```
always @(posedge clock) begin
  if (reset) begin
    cntReg <= 32'h0;
  end else if (_T_2) begin
    cntReg <= 32'h0;
  end else begin
    cntReg <= _T_1;
  end
end
end
```


Verilog Generation Summary

- ▶ Verilog is generated for synthesis
- ▶ We do not need to read it
- ▶ Just pins are interesting
- ▶ Additional clock and reset
- ▶ Pin names with additional io_

File Organization in Scala/Chisel

- ▶ A Scala file can contain several classes (and objects)
- ▶ For large classes use one file per class with the class name
- ▶ Scala has packages, like Java
- ▶ Use folders with the package names for file organization
- ▶ sbt looks into current folder and `src/main/scala/`
- ▶ Tests shall be in `src/test/scala/`

File Organization in Scala/Chisel

 

What is a Minimal Chisel Project?

- ▶ Scala class (e.g., `Hello.scala`)
- ▶ Build info in `build.sbt` for sbt:

```
scalaVersion := "2.12.13"
```

```
scalacOptions += Seq(  
  "-feature",  
  "-language:reflectiveCalls",  
)
```

```
resolvers += Seq(  
  Resolver.sonatypeRepo("releases")  
)
```

Minimal Chisel Project Cont.


```
// Chisel 3.5
addCompilerPlugin("edu.berkeley.cs" %
    "chisel3-plugin" % "3.5.0" cross
    CrossVersion.full)
libraryDependencies += "edu.berkeley.cs" %%
    "chisel3" % "3.5.0"
libraryDependencies += "edu.berkeley.cs" %%
    "chiseltest" % "0.5.0"
```

Show It

- ▶ The absolute minimum is two files
 - ▶ `build.sbt`
 - ▶ A single `.scala` file


Sequential Building Blocks

 - ▶ Contain a register
- ▶ Plus combinational circuits



```
val q = RegNext(d)
```


Register With Reset

 

```
val valReg = RegInit(0.U(4.W))
```


```
valReg := inVal
```

 Timing Diagram of the Register with Reset



- ▶ Also called waveform diagram
- ▶ Logic function over time
- ▶ Can be used to describe a circuit function
- ▶ Useful for debugging

Register with Enable

 

- ▶ Only when enable true is a value is stored

```
val enableReg = Reg(UInt(4.W))
```

```
when (enable) {  
  enableReg := inVal  
}
```


A Register with Reset and Enable


- ▶ We can combine initialization and enable

```
val resetEnableReg = RegInit(0.U(4.W))  
  
when (enable) {  
    resetEnableReg := inVal  
}
```

- ▶ A register can also be part of an expression
- ▶ What does the following circuit do?

```
val risingEdge = din & !RegNext(din)
```

A Register with an Adder is a Counter

 

- ▶ Is a free running counter
- ▶ 0, 1, ... 14, 15, 0, 1, ...

```
val cntReg = RegInit(0.U(4.W))
```

```
cntReg := cntReg + 1.U
```


A Counter with a Mux

```
val cntReg = RegInit(0.U(8.W))
```

```
cntReg := Mux(cntReg === 9.U, 0.U, cntReg + 1.U)
```

- ▶ This counter counts from 0 to 9
- ▶ And starts from 0 again after reaching 9
 - ▶ Starting from 0 is common in computer engineering
- ▶ A counter is the hardware version of a *for loop*
- ▶ Often needed

Counting Events

 

```
val cntEventsReg = RegInit(0.U(4.W))  
when(event) {  
  cntEventsReg := cntEventsReg + 1.U  
}
```

Counting Up and Down

▶ Up:

```
val cntReg = RegInit(0.U(8.W))  
  
cntReg := cntReg + 1.U  
when(cntReg === N) {  
    cntReg := 0.U  
}
```

▶ Down:

```
val cntReg = RegInit(N)  
  
cntReg := cntReg - 1.U  
when(cntReg === 0.U) {  
    cntReg := N  
}
```

Common Acronyms

- ADC** analog-to-digital converter
- ALU** arithmetic and logic unit
- ASIC** application-specific integrated circuit
- Chisel** constructing hardware in a Scala embedded language
- CISC** complex instruction set computer
- CRC** cyclic redundancy check
- DAC** digital-to-analog converter
- DFF** D flip-flop, data flip-flop
- DMA** direct memory access
- DRAM** dynamic random access memory
- FF** flip-flop

Common Acronyms II

FIFO first-in, first-out

FPGA field-programmable gate array

HDL hardware description language

HLS high-level synthesis

IC instruction count

IDE integrated development environment

IO input/output

ISA instruction set architecture

JDK Java development kit

JIT just-in-time

JVM Java virtual machine

LC logic cell

Common Acronyms III

LRU least-recently used

MMIO memory-mapped IO

MUX multiplexer

OO object oriented

RISC reduced instruction set computer

SDRAM synchronous DRAM

SRAM static random access memory

TOS top-of stack

UART universal asynchronous receiver/transmitter

VHDL VHSIC hardware description language

VHSIC very high speed integrated circuit

Lab Today

- ▶ Components and Small Sequential Circuits
- ▶ [Lab 3 Page](#)
- ▶ Each exercise contains a test, which initially fails
- ▶ `sbt test` runs them all
 - ▶ To just run a single test, run e.g.,
`sbt "testOnly SingleTest"`

When all tests succeed you are (almost) done ;-)

- ▶ Additional some drawing exercise
- ▶ Do them, they will be part of the exam!

Summary

- ▶ Vending machine is your final project
- ▶ The vending machine and the report are part of your grade
- ▶ A digital circuit is organized in components
- ▶ Components have ports with directions
- ▶ Sequential circuits are combinations of registers with combinational circuits