

# Finite State Machine with Datapath

Martin Schoeberl

Technical University of Denmark  
Embedded Systems Engineering

March 14, 2024

# Overview

- ▶ Review Vec
- ▶ Counter based circuits
- ▶ Finite-state machines (FSMs)
- ▶ FSM with Datapath
- ▶ Input processing

## Last Lab

- ▶ A table to describe a 7-segment decoder and drive it
- ▶ Did you finish the exercises?
- ▶ Did you run it on your Basys3 board?
- ▶ Show it a TA for a tick!

# TinyTapeout

- ▶ Do a *real* chip within DE 2
- ▶ a multi-project waver (within a multi-project waver)
- ▶ I can pay a few projects
- ▶ TinyTapeout
- ▶ Chisel template


# Vectors

- ▶ A powerful abstraction
- ▶ Let us repeat it today
- ▶ A vector (`Vec`) is an indexable collection
- ▶ Similar to an array in Java
- ▶ Selecting an element for read is a multiplexer
- ▶ Selecting an element to write is an input to a multiplexer or a register enable
- ▶ Bundles are constructs to structure data
- ▶ Similar to a class in Java or a record in C/VHDL
 
# A Vector is a Multiplexer

- ▶ Following code is a 3:1 multiplexer

```
val m = Wire(Vec(3, UInt(8.W)))  
m(0) := x  
m(1) := y  
m(2) := z  
val muxOut = m(select)
```



# A Vector of Registers

- ▶ Following code shows vectors and registers in action


```
val vReg = Reg(Vec(3, UInt(8.W)))
```

```
val dout = vReg(rdIdx)
```

```
vReg(wrIdx) := din
```

- ▶ Can you draw the schematic?


# Schematic of the Reg of Vec

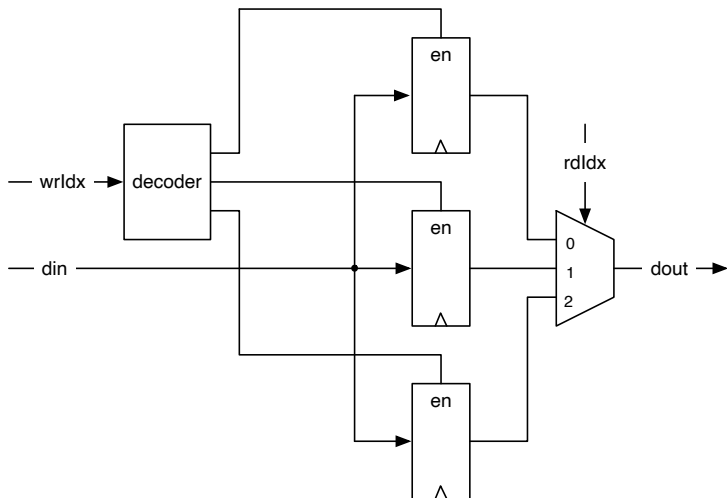


 
# Generating Timing with Counters

- ▶ Generate a tick at a lower frequency
- ▶ We used it in Lab 1 for the blinking LED
- ▶ You needed it for last week's lab
- ▶ We will use it again in next week's lab
- ▶ Use it for driving the display multiplexing at 1 kHz



# The Tick Generation

```
val tickCounterReg = RegInit(0.U(32.W))
val tick = tickCounterReg === (N-1).U

tickCounterReg := tickCounterReg + 1.U
when (tick) {
    tickCounterReg := 0.U
}
```


## Using the Tick

- ▶ A counter running at a *slower frequency*
- ▶ By using the tick as an enable signal

```
val lowFrequCntReg = RegInit(0.U(4.W))
when (tick) {
    lowFrequCntReg := lowFrequCntReg + 1.U
}
```

# The *Slow Counter*

- ▶ Incremented every tick

 

## What is the Use of This *Slow* Counter?


- ▶ This will be your lab exercise next week
- ▶ For the display multiplexing
- ▶ Then you need to generate a timing of 1 kHz (1 ms)

# Finite-State Machine (FSM)


- ▶ Has a register that contains the state
- ▶ Has a function to computer the next state
  - ▶ Depending on current state and input
- ▶ Has an output depending on the state
  - ▶ And maybe on the input as well
- ▶ Every synchronous circuit can be considered a finite state machine
- ▶ However, sometimes the state space is a little bit too large
 
# Basic Finite-State Machine

- ▶ A state register
- ▶ Two combinational blocks
  - ▶ Next state logic
  - ▶ Output logic



## State Diagrams are Convenient

 


- ▶ States and transitions depending on input values
- ▶ Example is a simple alarm FSM
- ▶ Nice visualization
- ▶ Will not work for large FSMs



 
# A Mealy FSM

- ▶ Similar to the former FSM
- ▶ Output also depends in the input
- ▶ Output is *faster*
- ▶ Less composable as we may have combinational circles



 
# The Mealy FSM for the Rising Edge

- ▶ Output is also part of the transition arrows




# State Diagram for the Moore Rising Edge Detection

- ▶ We need three states

 
 
# Comparing with a Timing Diagram

- ▶ Moore is delayed by one clock cycle compared to Mealy



# What is Better?

- ▶ It depends ;-)
- ▶ Moore is on the save side
- ▶ Moore is composable
- ▶ Mealy has *faster* reaction
- ▶ Both are tools in you toolbox
- ▶ Keep it simple with your vending machine and use a Moore FSM

# Working Break

- ▶ 20' break
- ▶ We are half way through the course
- ▶ Therefore, a midterm [evaluation](#)
- ▶ Send also on Slack (from the slide sources or the website)

# FSM with Datapath

- ▶ A type of computing machine
- ▶ Consists of a finite-state machine (FSM) and a datapath
- ▶ The FSM is the master (the controller) of the datapath
- ▶ The datapath has computing elements
  - ▶ E.g., adder, incrementer, constants, multiplexers, ...
- ▶ The datapath has storage elements (registers)
  - ▶ E.g., sum of money payed, count of something, ...

# FSM-Datapath Interaction


- ▶ The FSM controls the datapath
  - ▶ For example, add 2 to the sum
- ▶ By controlling multiplexers
  - ▶ For example, select how much to add
  - ▶ Not adding means selecting 0 to add
- ▶ Which value goes where
- ▶ The FSM logic also depends on datapath output
  - ▶ Is there enough money payed to release a can of soda?
- ▶ FSM and datapath interact



# Popcount Example


- ▶ An FSMD that computes the popcount
- ▶ Also called the Hamming weight
- ▶ Compute the number of '1's in a word
- ▶ Input is the data word
- ▶ Output is the count
- ▶ Code available at [PopulationCount.scala](#)

# Popcount Block Diagram

 

 
# Popcount Connection

- ▶ Input `din` and output `popCount`
- ▶ Both connected to the datapath
- ▶ We need some handshaking
- ▶ For data input and for count output



 
# Popcount Handshake

- ▶ We use a ready-valid handshake
- ▶ When data is available valid is asserted
- ▶ When the receiver can accept data ready is asserted
- ▶ Transfer takes place when both are asserted
- ▶ Draw the ready/valid handshake on the black board




# The FSM

 

- ▶ A Very Simple FSM
- ▶ Two transitions depend on input/output handshake
- ▶ One transition on the datapath output

# The Datapath

 

# Let's Explore the Code

- ▶ In `PopulationCount.scala`

# Usage of an FSMD


- ▶ Maybe the main part of your vending machine is an FSMD?



# Input Processing

- ▶ Input signals are not synchronous to the clock
- ▶ May violate setup and hold time of a flip-flop
- ▶ Can lead to metastability
- ▶ Signals need to be *synchronized*
- ▶ Using two flip-flops
- ▶ Metastability cannot be avoided
- ▶ Assumption is:
  - ▶ First flip-flop may become metastable
  - ▶ But will resolve within the clock period
- ▶ Input can arrive at different clock cycles at different places

# Input Synchronizer

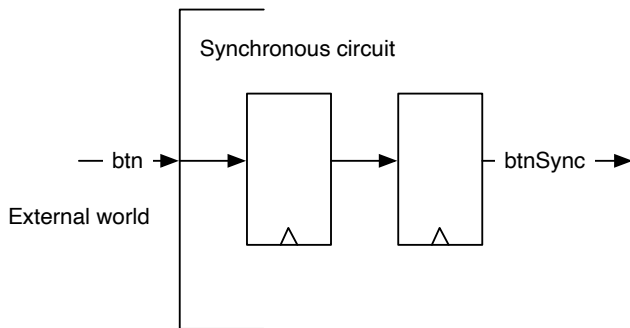


```
val btnSync = RegNext(RegNext(btn))
```

# Bouncing Buttons

- ▶ Buttons and switches need some time to transition between on and off
- ▶ May bounce between the two values
- ▶ Without processing we detect more than one event
- ▶ Solution is to filter out bouncing
  - ▶ Can be done electrically (R + C + Schmitt trigger)
  - ▶ That is why you have the extra PCB with the buttons
  - ▶ But we can also do this digitally
  - ▶ You can then drop your additional board ;-)
- ▶ Assume bouncing time  $t_{bounce}$
- ▶ Sample at a period  $T > t_{bounce}$
- ▶ Only use sampled signal

# Sampling for Debouncing

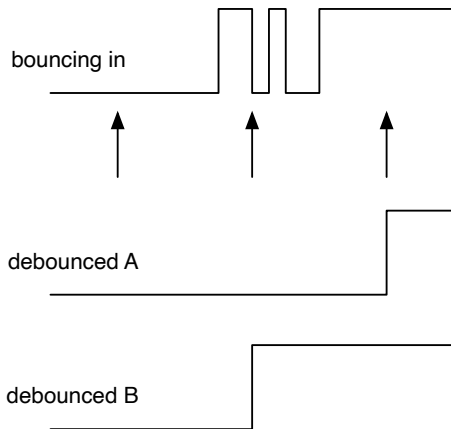

## Sampling for Debouncing

```
val fac = 1000000000/100

val btnDebReg = Reg(Bool())

val cntReg = RegInit(0.U(32.W))
val tick = cntReg === (fac-1).U

cntReg := cntReg + 1.U
when (tick) {
  cntReg := 0.U
  btnDebReg := btnSync
}
```

- ▶ We already know how to do this!
- ▶ Just generate timing with a counter
- ▶ We sample at 100 Hz (bouncing below 10 ms)

# Agile Hardware Design Course

- ▶ Advanced Chisel
- ▶ by Scott Beamer from UC Santa Cruz
- ▶ Includes executable slides
- ▶ <https://classes.soe.ucsc.edu/cse228a/Winter23/>
- ▶ Includes Videos
- ▶ I will do a similar course for the new CE Bachelor

# Today's Lab

- ▶ Paper & pencil exercises (see course website)
- ▶ Exercises on FSMs
- ▶ From the Dally book
- ▶ Just sketch the Chisel code
- ▶ On paper or in a plain text editor
- ▶ As usual, show and discuss your solution with a TA
- ▶ Also finish you lab from last week and get the tick

# Summary

- ▶ Counters are used to generate timing
- ▶ An FSM can control a datapath, which is an FSMD
- ▶ An FSMD is a computing machine
- ▶ Input needs to be processed (synchronize, maybe debounce)