

Refactor of State Machines

Martin Schoeberl

Technical University of Denmark
Embedded Systems Engineering

March 21, 2024

TODO

- ▶ Show studie start slides


Outline

- ▶ Repeat finite-state machine with datapath
- ▶ Factoring of finite-state machines
- ▶ Functions and parameters
- ▶ Reset input

Popcount Example


- ▶ An FSM_D that computes the popcount
- ▶ Also called the Hamming weight
- ▶ Compute the number of '1's in a word
- ▶ Input is the data word
- ▶ Output is the count
- ▶ Code available at [PopulationCount.scala](#)

Popcount Block Diagram

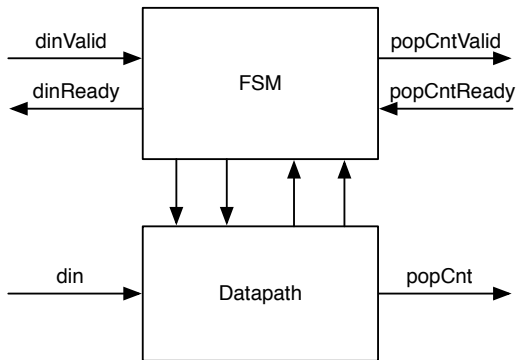


Popcount Connection

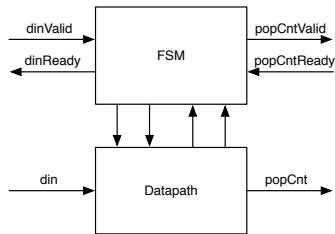- ▶ Input `din` and output `popCount`
- ▶ Both connected to the datapath
- ▶ We need some handshaking
- ▶ For data input and for count output




Popcount Handshake

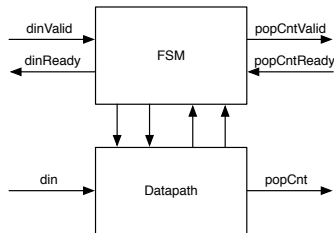- ▶ We use a ready-valid handshake
- ▶ When data is available valid is asserted
- ▶ When the receiver can accept data ready is asserted
- ▶ Transfer takes place when both are asserted




The FSM

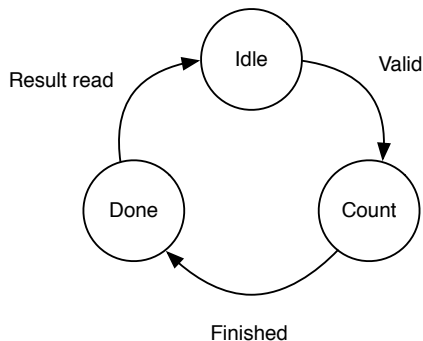

- ▶ A Very Simple FSM
- ▶ Two transitions depend on input/output handshake
- ▶ One transition on the datapath output

The Datapath

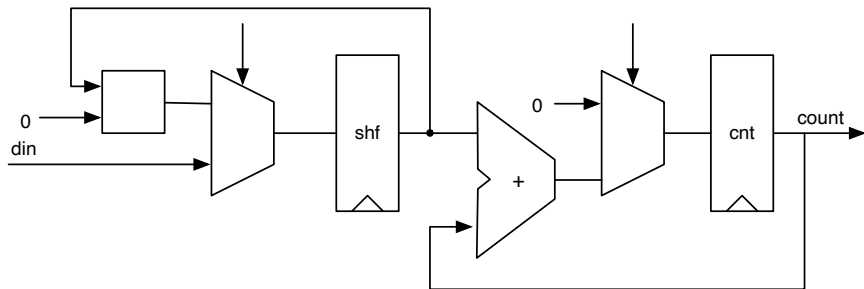

Let's Explore the Code

- ▶ In `PopCount.scala`

Usage of an FSMD

- ▶ Maybe the main part your vending machine is an FSMD?

FSM with Datapath

- ▶ A type of computing machine
- ▶ Consists of a finite-state machine (FSM) and a datapath
- ▶ The FSM is the master (the controller) of the datapath
- ▶ The datapath has computing elements
 - ▶ E.g., adder, incrementer, constants, multiplexers, ...
- ▶ The datapath has storage elements (registers)
 - ▶ E.g., sum of money payed, count of something, ...

FSM-Datapath Interaction

- ▶ The FSM controls the datapath
 - ▶ For example, add 2 to the sum
- ▶ By controlling multiplexers
 - ▶ For example, select how much to add
 - ▶ Not adding means selecting 0 to add
- ▶ Which value goes where
- ▶ The FSM logic also depends on datapath output
 - ▶ Is there enough money payed to release a can of soda?
- ▶ FSM and datapath interact

Factoring FSMs

- ▶ Divide a big problem into several smaller problems
- ▶ Splitting a FSM into two or more
 - ▶ Simplify the design
- ▶ FSMs communicate via logic signals
 - ▶ FSM provides input controls signals to another
 - ▶ FSM senses output from another

Specification Of a Light Flasher

- ▶ Inputs: `start`
- ▶ Outputs: `light`
- ▶ Operation:
 - ▶ When `in = 1`, FSM goes through 5 sequences:
 - ▶ On-Off-On-Off-On
 - ▶ Each On sequence (`flash`):
 - ▶ `out = 1`
 - ▶ 6 cycles long
 - ▶ Each Off sequence (`space`):
 - ▶ `out = 0`
 - ▶ 4 cycles long
 - ▶ After 5 sequences, FSM goes back to `off` state to wait for new input

Light Flasher State Diagram

- ▶ Example from Dally, Chapter 17
- ▶ Copyright figure, so show it from older slides


Specification Change

- ▶ We have a flat FSM with 27 states
 - ▶ 27 `is(state)` statements
- ▶ If we change the specification to
 - ▶ 12 cycles for each flash
 - ▶ 4 flashes
 - ▶ 7 cycles between flashes
 - ▶ Complete change of `switch` statement
 - ▶ Now 70 `is` statements!
- ▶ This does not scale

Factor Light Flasher

- ▶ Factor out counting on and off intervals
 - ▶ Into a timer
 - ▶ Reduces 6 and 4 states sequences into two single states
- ▶ Results in
 - ▶ a master FSM and
 - ▶ a timer FSM
- ▶ Simplifies FSMs
- ▶ Allows easier change of interval lengths

Factored Light Flasher

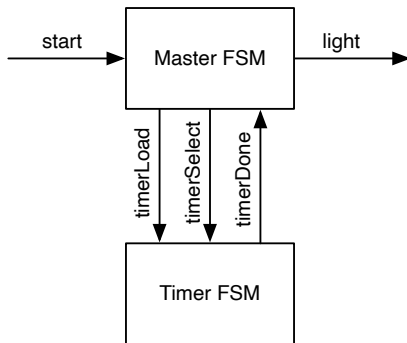

- ▶ Time loads value 5 or 3, based in `timerSelect`

Timer Specification

- ▶ Two inputs
 - ▶ `timerLoad` to load the down counter
 - ▶ `timerSelect` to select between 6 and 4 cycles counting
- ▶ Output
 - ▶ `timerDone` is 1 when counter has completed the countdown
 - ▶ Remains asserted until counter reloaded
- ▶ Counter can be (re)loaded in any state
 - ▶ When not loaded it counts down to zero
- ▶ Similar to the timer we looked at two weeks ago

The Timer FSM

```
val timerReg = RegInit(0.U)
timerDone := timerReg === 0.U

// Timer FSM (down counter)
when(!timerDone) {
  timerReg := timerReg - 1.U
}
when (timerLoad) {
  when (timerSelect) {
    timerReg := 5.U
  } .otherwise {
    timerReg := 3.U
  }
}
```

The Master FSM

- ▶ Show in IntelliJ
- ▶ Run test and show waveform


Result of Refactoring

- ▶ State of original flat FSM has been separated
- ▶ The part of cycle counting in the counter
- ▶ Part flash or space in master FSM
- ▶ Represent original 27 states in just two 6 states FSMs
- ▶
- ▶ BTW: the master FSM is a Mealy FSM

Still Redundancy in FSM

- ▶ `flash1`, `flash2`, and `flash3` same function
- ▶ `space1` and `space2` same function
- ▶ Refactor number of remaining flashes
- ▶ Master FSM states: `off`, `flash`, and `space`

Factor out “flash number”

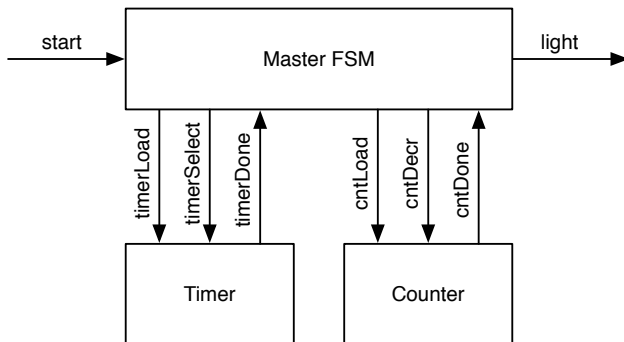

Counter

```
val cntReg = RegInit(0.U)
cntDone := cntReg === 0.U

// Down counter FSM
when(cntLoad) { cntReg := 2.U }
when(cntDecr) { cntReg := cntReg - 1.U }
```

- ▶ Loaded with 2 for 3 flashes
- ▶ Counts the *remaining* flashes

Code of Flasher2

- ▶ Show in IntelliJ
- ▶ Run test and show waveform

Benefits of Refactored Solution

- ▶ Master FSM has just three states: `off`, `flash`, and `space`
- ▶ Change of intervals or number of flashes needs no change in the FSM
- ▶ Smaller components are easier to read and simpler to test individually

Usage in your VM


- ▶ Maybe factor out the edge detection for the button(s)
- ▶ Use a timer for more advanced user interface
 - ▶ Blinking LED on some error
 - ▶ Write text as a banner in the 7-segment display
 - ▶ ...

10' Break

Input Processing


- ▶ Input signals are not synchronous to the clock
- ▶ May violate setup and hold time of a flip-flop
- ▶ Can lead to metastability
- ▶ Signals need to be *synchronized*
- ▶ Using two flip-flops
- ▶ Debouncing the input with subsampling
- ▶ Input signal may be noisy (spikes)

Input Synchronizer

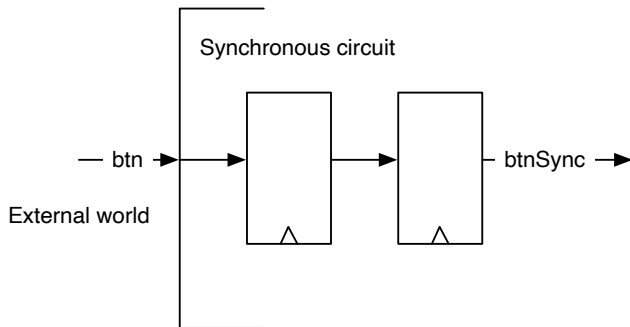

```
val btnSync = RegNext(RegNext(btn))
```



Sampling for Debouncing

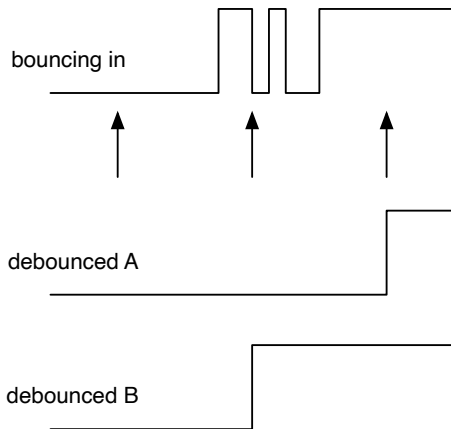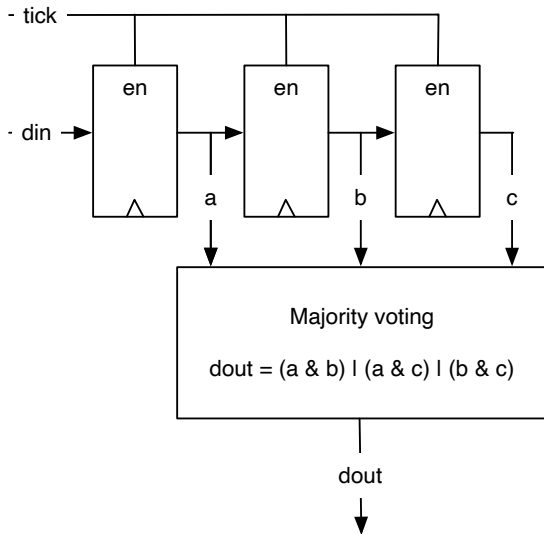

Noisy Input Signal

- ▶ Sometimes input may be noisy
- ▶ May contain spikes
- ▶ Filtering with majority voting
- ▶ Majority voting of the sampled input signal
- ▶ However, this is seldom needed
- ▶ Not for the buttons you have

Majority Voting



Majority Voting

```
val shiftReg = RegInit(0.U(3.W))
when (tick) {
    // shift left and input in LSB
    shiftReg := shiftReg(1, 0) ## btnDebReg
}
// Majority voting
val btnClean = (shiftReg(2) & shiftReg(1)) |
    (shiftReg(2) & shiftReg(0)) | (shiftReg(1) &
    shiftReg(0))
```

Detecting the Press Event

- ▶ Edge detection
- ▶ You have seen this before
- ▶ Just to complete the input processing

```
val risingEdge = btnClean & !RegNext(btnClean)
```

```
// Use the rising edge of the debounced and  
// filtered button to count up
```

```
val reg = RegInit(0.U(8.W))  
when (risingEdge) {  
    reg := reg + 1.U  
}
```

Display Multiplexing

- ▶ Saving of pins in the FPGA
- ▶ Switch between the four digits at around 1 kHz
- ▶ Switch *faster* in simulation
- ▶ Show [schematics](#)
- ▶ Also includes a display simulation for those without an FPGA
- ▶ [Lab 6](#)
- ▶ Sketch needed hardware on black board

Functions

- ▶ Circuits can be encapsulated in functions
- ▶ Each *function call* generates hardware
- ▶ A function is defined with `def name`
- ▶ Similar to methods in Java

```
def adder (x: UInt, y: UInt) = {  
    x + y  
}
```

```
val x = adder(a, b)  
// another adder  
val y = adder(c, d)
```

More Function Examples

- ▶ Functions can also contain registers
- ▶ Simple functions can be a single line

```
def delay(x: UInt) = RegNext(x)
```

```
def rising(d: Bool) = d && !RegNext(d)  
val edge = rising(cond)
```


The Counter as a Function

- ▶ Longer functions in curly brackets
- ▶ Last value is the return value

```
// This function returns a counter  
def genCounter(n: Int) = {  
  val cntReg = RegInit(0.U(8.W))  
  cntReg := Mux(cntReg == n.U, 0.U, cntReg +  
    1.U)  
  cntReg  
}
```

```
// now we can easily create many counters  
val count10 = genCounter(10)  
val count99 = genCounter(99)
```

Functional Abstraction

- ▶ Functions for repeated pieces of logic
- ▶ May contain state
- ▶ Functions may return *hardware*
- ▶ More lightweight than a Module

Parameterization

```
class ParamChannel(n: Int) extends Bundle {  
  val data = Input(UInt(n.W))  
  val ready = Output(Bool())  
  val valid = Input(Bool())  
}
```

```
val ch32 = new ParamChannel(32)
```

- ▶ Bundles and modules can be parametrized
- ▶ Pass a parameter in the constructor

A Module with a Parameter

```
class ParamAdder(n: Int) extends Module {  
  val io = IO(new Bundle{  
    val a = Input(UInt(n.W))  
    val b = Input(UInt(n.W))  
    val c = Output(UInt(n.W))  
  })  
  
  io.c := io.a + io.b  
}
```

- ▶ Parameter can also be a Chisel type

Use the Parameter

```
val add8 = Module(new ParamAdder(8))  
val add16 = Module(new ParamAdder(16))
```

- ▶ Can be used for the display multiplexing configuration
- ▶ Different maximum value for the counter for the simulation and for the FPGA

Combine Input Processing with Functions

- ▶ Using small functions to abstract the processing
- ▶ [Debounce.scala](#)

Reset is an Asynchronous Signal

- ▶ Needs a input synchronizer
- ▶ Usually hidden in Chisel, but easy to access
- ▶ Do the reset synchronizer at the top level module

```
class SyncReset extends Module {  
  val io = IO(new Bundle() {  
    val value = Output(UInt())  
  })  
  
  val syncReset = RegNext(RegNext(reset))  
  val cnt = Module(new WhenCounter(5))  
  cnt.reset := syncReset  
  
  io.value := cnt.io.cnt  
}
```

DTU Chip Day

- ▶ Program is [online](#)
- ▶ Register [here](#)
- ▶ Free sandwiches and free beer ;-)

Summary

- ▶ Divide a bigger problem into smaller ones
 - ▶ Easier to design
 - ▶ Easier to test
 - ▶ Sometimes only feasible solution
- ▶ Factoring state machines
 - ▶ Separate state into multiple 'orthogonal' state variables
 - ▶ Each is simpler to handle (fewer states)
 - ▶ "Factors out" repetitive sequences
 - ▶ Hierarchical structure