# Interfacing and Memory

Martin Schoeberl

Technical University of Denmark Embedded Systems Engineering

April 10, 2025

## Overview

Repeat FSMD (for the vending machine)

- I have (earlier) seen some intermix of FSM and datapath
- Works only for small designs
- GoL: a highly parallel example (including co-simulation)
- Interfaces
- Memory (intern and extern)
- Busses
- Lab is the vending machine

#### I have seen similar code (not this year)

```
when(io.coin2) {
   sum := sum + 2.U
} .elsewhen(io.coin5) {
   sum := sum + 5.U
}
```

- This may work for tiny projects
- This style does not scale for larger designs
- I recommend using an FSM + datapath
  - Split responsibility
  - Can be individually tested
  - Can be developed in parallel

# Usage of an FSMD

#### Of course for your VM

- The VM is a simple processor
- But not Turing complete
- Can only process coins of 2 and 5
- Have the FSM and the data path in two Modules
- An FSMD can be used to build a processor
- Fine for simple processors
- E.g., Lipsi
- Pipelined processor topic of
  - Computer Architecture Engineering (02155)

## Test the FSMD for the VM

- This is the main part your vending machine
- Can be design and tested just with Chisel testers (no FPGA board needed)
- See the given tester
  - Sets the price to 7
  - Adds two coins (2 and 5)
  - Presses the buy button
- Extend the test along the development
  - Remember test driven development?
  - Maybe test developer and FSMD developer are not always the same person

# **Testing Your Vending Machine**

- Write (unit) tests for each component/module
- E.g., one for the data path, one for the state machine
- Then one (integration) test for the top-level component/module
- Maybe do some extreme programming (XP)
  - Write the test first
  - Then the code of the component
  - The test can serve as a specification
  - We can do agile hardware development

#### Game of Live

#### Conway's Game of Life

- Any live cell with two or three live neighbors survives.
- Any dead cell with three live neighbors becomes a live cell.
- All other live cells die in the next generation. Similarly, all other dead cells stay dead.

#### Game of Live

- You did an implementation in Java
- The problem is highly parallel
- I will show you a Chisel (and Java) implementation
- FPGA version is extremely fast compared to the Java implementation
- It contains co-simulation
- https://github.com/schoeberl/game-of-live

# Performance Comparison

		Execution time (us)			FPGA Speedup	
World	Cells	Mac	Rasperry	FPGA	Mac	Rasperry
10x10	100	0.10	1.783	0.0040	25	445
20x20	400	0.33	5.137	0.0040	82	1284
30x30	900	0.70	9.965	0.0041	170	2430
40x40	1600	1.21	17.212	0.0040	302	4302
50x50	2500	1.81	25.204	0.0044	411	5728
60x60	3600	2.76	37.822	0.0045	613	8404
70x70	4900	3.54	57.665	0.0040	884	14416
80x80	6400	4.81	64.396	0.0047	1023	13701
90x90	8100	6.50	81.309	0.0045	1444	18068
100x100	10000	7.51	109.964	0.0048	1564	22909

# Memory

Registers are storage elements == memory

- Just use a Reg of a Vec
- This is 1 KiB of memory

```
val memoryReg = Reg(Vec(1024, UInt(8.W)))
// writing into memory
memoryReg(wrAddr) := wrData
// reading from the memory
val rdData = memoryReg(rdAddr)
```

Simple, right?

But is this a good solution?

# A Flip-Flop

- Remember the circuit of a register (flip-flop)?
- Two latches: master and slave
- One (enable) latch can be built with 4 NAND gates
- a NAND gate needs 4 transistors, an inverter 2 transistors
- A flip-flop needs 36 transistors (for a single bit)
- Can we do better?

# A Memory Cell

- A single bit can be stored in 6 transistors
- That is how larger memories are built
- FPGAs have this type of on-chip memories
- Usually many of them in units of 2 KiB or 4 KiB
- We need some Chisel code to represent it
- More memory needs an external chip
- Then we need to interface this memory from the FPGA

# **SRAM Memory**

- RAM stands for random access memory
- SRAM stands for static RAM
- There is also something called DRAM for dynamic RAM
  - Uses a capacitor and a transistor
  - DRAM is smaller than SRAM
  - But needs refreshes
  - Different technology than technology for logic
- All on-chip memory is SRAM (today)

# Memory Interface

Interface

- Address input (e.g., 10 bits for 1 KiB)
- Write signal (e.g., we)
- Data input
- Data output
- May share pins for the data input and output (tri-state)
- May have read and write addresses
  - A so-called dual ported memory
  - Can do a read and a write in the same clock cycle

# **On-Chip Memory**

- SRAM by itself is asynchronous
- No clock, just the correct timing
- Apply the address and after some time the data is valid
- But one can add input registers, which makes it a synchronous SRAM
- Current FPGAs have synchronous memories only
- This means the result of a read is available one clock cycle after the address is given

This is different from the use of flip-flops (Reg(Vec(..)))

FPGAs usually have dual-ported memories

# Synchronous Memory



#### Use of a Chisel SyncReadMem

```
class Memory() extends Module {
  val io = IO(new Bundle {
    val rdAddr = Input(UInt(10.W))
    val rdData = Output(UInt(8.W))
    val wrAddr = Input(UInt(10.W))
    val wrData = Input(UInt(8.W))
    val wrEna = Input(Bool())
 })
 val mem = SyncReadMem(1024, UInt(8.W))
  io.rdData := mem.read(io.rdAddr)
  when(io.wrEna) {
    mem.write(io.wrAddr, io.wrData)
  }
}
```

# **Read-During-Write**

What happens when one writes to and reads from the same address?

- Which value is returned?
- Three possibilities:
  - 1. The newly written value
  - 2. The old value
  - 3. Undefined (mix of old and new)
- Depends on technology, FPGA family, ...
- We want to have a defined read-during-write
- We add hardware to *forward* the written value

# Condition for Forwarding

- If read and write addresses are equal
- If write enable is true
- Multiplex the output to take the new write value instead of the (old) read value
- Delay that forwarded write value to have the same timing

## Memory with Forwarding



## Forwarding in Chisel

```
val mem = SyncReadMem(1024, UInt(8.W))
val wrDataReg = RegNext(io.wrData)
val doForwardReg = RegNext(io.wrAddr ===
   io.rdAddr && io.wrEna)
val memData = mem.read(io.rdAddr)
when(io.wrEna) {
  mem.write(io.wrAddr, io.wrData)
}
io.rdData := Mux(doForwardReg, wrDataReg,
   memData)
```

# **External Memory**

- On-chip memory is limited
- We can add an external memory chip
  - Is cheaper than FPGA on-chip memory
- Sadly the Basys 3 board has no external memory
- Simple memory is an asynchronous SRAM

#### **External SRAM**

- ▶ We *buy* a CY7C1041CV33
- Let us look into the data sheet

# Interfacing the SRAM

- FPGA output drives address, control, and data (sometimes)
- FPGA reads data
- The read signal is asynchronous to the FPGA clock
- Do we need an input synchronizer?

# Synchronous Interface

- Logic is synchroous
- Memory is asynchronous
  - How to interface?
- Output signals
  - Generate timing with synchronous circuit
  - Small FSM
- Asynchronous input signale
  - Usually 2 register for input synchronization
  - Really needed for the SRAM interface?
  - We would loose 2 clock cycles

#### SRAM Read

- Asynchronous timing definition (data sheet)
- But, we know the timing and we trigger the SRAM address from our synchronous design
- No need to use synchronization registers
- Just get the timing correct
- Draw the example
  - Address SRAM data
  - Relative to the FPGA clock

# **Read Timing Continued**

Add all time delays

- Within FPGA
- Pad to pin
- PCB traces
- SRAM read timing
- PCB traces back
- Pin to pad
- Into FPGA register

Setup and hold time for FPGA register

# Connecting to the World

#### Logic in the FPGA

- Described in Chisel
- Abstracting away electronic properties
- Interface to the world
  - Simple switches and LEDs
  - Did we think about timing?
- FPGA is one component of the system
- Need interconnect to
  - Write outputs
  - Read inputs
  - Connect to other chips

#### **Bus Interface**

- Memory interface can be generalized
- We use a so-called bus to connect several devices
- Usually a microprocessor connected to devices (memory, IO)
- The microprocessor is the master
- A bus is an interface definition
  - Logic and timing
  - Electrical interface
- Parallel or serial data
- Asynchronous or synchronous
  - But interface clock is usually not the logic clock

# **Bus Properties**

- Address bus and data bus
- Control lines (read and write)
- Several devices connected
  - Multiple outputs
  - Use tri-state to avoid multiple driver
- Single or multiple master
  - Arbitration for multiple master

# A Classic Microprocessor Bus



# Does This Work On-Chip?

- Just mapping that bus on-chip?
- Tri-state not so easy
- Wires are cheap
- Use dedicated connections and a Mux

# An On-Chip Bus



## Serial I/O Interface

Use only one wire for data transfer

- Bits are serialized
- That is where you need your shift register
- Shared wire or dedicated wires for transmit and receive
- Self timed
  - Serial UART (RS 232)
  - Ethernet
  - USB
- With a clock signal
  - SPI, I2C, ...

# RS 232

Old, but still common interface standard

- Was common in 90' in PCs
- Now substituted by USB
- Still common in embedded systems
- Your Basys 3 board has a RS 232 interface
- Standard defines
  - Electrical characteristics
  - '1' is negative voltage (-15 to -3 V)
  - '0' is positive voltage (+3 to +15 V)
  - Converted by a RS 232 driver to normal logic voltage levels

# Serial Transmission

Transmission consists of

- Start bit (low)
- 8 data bits
- Stop bit(s) (high)
- Common baud rate is 115200 bits/s



# RS 232 Interface

- How would we implement this?
- Baud rate is 115200 bit/s (ca. 10 us)
- Clock on Basys 3 is 100 MHz (10 ns)
- Output (transmit)
- Input (receive)
- Let us do it now together

# RS 232 Interface

Generate bit clock with with counter

- Like clock tick generation for display multiplexer
- Output (transmit)
  - Use shift register for parallel to serial conversion
  - Small FSM to generate start bit, data bits, and stop bits
- Input (receive)
  - Detect start with the falling edge of the start bit
  - Position into middle of start bit
  - Sample individual bits
  - Serial to parallel conversion with a shift register

# Chisel Code for RS 232

- More explanation can be found in section 11.2
- The code is in the Chisel book
- uart.scala
- Also see example usage in chisel-examples repo

### RS 232 on the Basys 3

- Basys 3 has an FTDI chip for the USB interface
- USB interface for FPAG programming
- But also provides a RS 232 to the FPGA
- You can talk with your laptop
- You have used it last week ago
- How did it go?

### Today's and next Lab

- Work on your Vending Machine
- As usual, show and discuss with a TA
- Get a tick from a TA when done. This is VERY important!
- Add features and show again to the TA
- Optional: Testing two given vending machines
- Next week (after Easter): full lab day!

# Summary

- Use an FSMD for the vending machine and simple processors
- Hardware can be highly parallel (GoL)
- We need to connect to the world
- FPGA (or any chip) is only part of a system
- Bus interface to external devices (e.g., memory)
- Serial interface to connect systems
  - E.g., your Basys 3 board to the laptop